

# **SWITCH LEVEL MODELING**



# Introduction



- ❑ The MOS transistor is the basic element around which a VLSI is built.
- ❑ Designers familiar with logic gates and their configurations at the circuit level may choose to do their designs using MOS transistors.
- ❑ Verilog has the provision to do the design description at the switch level using such MOS transistors, which is the theme of the present chapter.
- ❑ Switch level modeling forms the basic level of modeling digital circuits.
- ❑ The switches are available as primitives in Verilog

# MOS Switches

- The MOS switches are:

**cmos pmos nmos rcmos rpmos rnmos**

- These gates model unidirectional switches, that is, data flows from input to output and the data flow can be turned off by appropriately setting the control input(s).
- The pmos(p-type MOS transistor), nmos (n-type MOS transistor), rnmos ('r' stands for resistive) and rpmos switches have one output, one input and one control input.
- The basic syntax for an instantiation is:

```
gate_type [ instance_name ] ( OutputA , InputB , ControlC );
```

# a. BASIC SWITCH PRIMITIVES


**nmos** switch primitives

**nmos** (out, in, control);


**pmos** switch primitives

**pmos** (out, in, control);

| <b>pmos</b><br><b>rp mos</b> |   | Control |   |     |      | <b>nmos</b><br><b>rn mos</b> |   | Control |   |      |      |
|------------------------------|---|---------|---|-----|------|------------------------------|---|---------|---|------|------|
|                              |   | 0       | 1 | x   | z    |                              |   | 0       | 1 | x    | z    |
| Data                         | 0 | 0       | z | 0/z | 0/ z | Data                         | 0 | z       | 0 | 0/ z | 0/ z |
|                              | 1 | 1       | z | 1/z | 1/ z |                              | 1 | z       | 1 | 1/ z | 1/ z |
|                              | x | x       | z | x   | x    |                              | x | z       | x | x    | x    |
|                              | z | z       | z | z   | z    |                              | z | z       | z | z    | z    |

 

nmos switch

 

pmos switch

```
pmos P1 (BigBus, SmallBus, GateControl);  
rnmos RN1 (ControlBit, ReadyBit, Hold);
```

*The first instance instantiates a pmosswitch with instance name P1. The input to the switch is SmallBus and the output is BigBus and the control signal is GateControl*

## b. Resistive switches

- **nmos** and **pmos** represent switches of low impedance in the on-state.
- **rnmos** and **rpmos** represent the resistive counterparts of these respectively.

rnmos (output1, input1, control1);

rpmos (output2, input2, control2);

- It inserts a definite resistance between the input and the output signals but retains the signal value
- The rpmos and rnmos switches function as unidirectional switches; the signal flow is from the input to the output side.

# Strength level

- Output-side strength levels for different input-side strength values of rnmos, rpmos, and rcmos switches

| Input strength      | Output strength     |
|---------------------|---------------------|
| Supply – drive      | Pull – drive        |
| Strong – drive      | Pull – drive        |
| Pull – drive        | Weak – drive        |
| Weak – drive        | Medium – capacitive |
| Large – capacitive  | Medium – capacitive |
| Medium – capacitive | Small – capacitive  |
| Small – capacitive  | Small – capacitive  |
| High impedance      | High impedance      |

## c. CMOS SWITCH


- A CMOS switch is formed by connecting a PMOS and an NMOS switch in parallel – the input leads are connected together on the one side and the output leads are connected together on the other side.
- The CMOS switch is instantiated as shown below.

**cmos** csw (out, in, N\_control, P\_control );

```
(r)cmos [ instance_name ]  
        ( OutputA , InputB , NControl , PControl );
```



- The cmos and rcmos (resistive version of cmos) switches have one data output, one data input and two control inputs.
- The first terminal is the output, the second is the input, the third is the n channel control input and the fourth terminal is the p-channel control input.
- A cmos (rcmos) switch behaves exactly like a combination of a pmos (rpmos) and an nmos (rnmos) switch with common outputs and common inputs;

 

## 2. pullup and pulldown

- A MOS transistor functions as a resistive element when in the active state. Realization of resistance in this form takes less silicon area in the IC as compared to a resistance realized directly.
- pullup and pulldown represent such resistive elements.

**pullup (x);**

- Here net x is pulled up to the supply1 through a resistance.

**pulldown(y);**

- pulls y down to the supply0 level through a resistance.
- The pullup and pulldown primitives can be used as loads for switches or to connect the unused input ports to VCC or GND, respectively.

# 3. Bidirectional Switches

- The bidirectional switches are:  
**tran rtran tranif0 rtranif0 tranif1 rtranif1**
- These switches are bidirectional, that is, data flows both ways and there is no delay when data propagates through the switches.
- The last four switches can be **turned off** by setting a **control signal** appropriately.
- The tran and rtran switches **cannot be turned off**.
- The syntax for instantiating a tran or a rtran (resistive version of tran) switch is:

```
(r)tran [ instance_name ] ( SignalA , SignalB );
```

- ❑ The terminal list has only two terminals and data flows unconditionally both ways, that is, from SignalA to SignalB and vice versa.
- ❑ The syntax for instantiating the other bidirectional switches is:

```
gate_type [ instance_name ] ( SignalA , SignalB , ControlC );
```

- The first two terminals are the bidirectional terminals, that is, data flows from SignalA to SignalB and vice versa.
- The third terminal is the control signal. If ControlC is 1 for tranif0 and rtranif0, and 0 for tranifl and rtranifl, the bidirectional data flow is disabled.
- For the resistive switches(rtran, rtranif0 and rtranifl), the strength of the signal reduces when it passes through the switch.

# Primitives Supported by Verilog

| COMBINATIONAL LOGIC GATES |                    |                   | SWITCH-LEVEL PRIMITIVES |                |                             |
|---------------------------|--------------------|-------------------|-------------------------|----------------|-----------------------------|
| Multi-input gates         | Multi-output gates | Three-state gates | MOS transistor switches | MOS Pull gates | MOS Bi-directional switches |
| and                       | buf                | bufif0            | nmos                    | pullup         | tran                        |
| nand                      | not                | bufif1            | pmos                    | pulldown       | tranif0                     |
| or                        |                    | notif0            | cmos                    |                | tranif1                     |
| nor                       |                    | <del>notif0</del> | rnmos                   |                | rtran                       |
| xor                       |                    |                   | rpmos                   |                | rtranif0                    |
| xnor                      |                    |                   | rcmos                   |                | rtranif1                    |

↓  
notif1

# Power and Ground

- ❑ The power ( $V_{dd}$ , logic 1) and Ground ( $V_{ss}$ , logic 0) sources are needed when transistor level circuits are designed.
- ❑ Power and ground sources are defined with keywords `supply1` and `supply0`.
- ❑ Sources of type `supply1` are equivalent to  $V_{dd}$  in circuits and place a logical 1 on a net.
- ❑ Sources of the type `supply0` are equivalent to ground or  $V_{ss}$  and place a logical 0 on a net.
- ❑ Both `supply1` and `supply0` place logical 1 and 0 continuously on nets throughout the simulation.

# Example:

- `supply1, supply0`

```
supply1 vdd;  
supply0 gnd;
```

```
assign a = vdd; //Connect a to vdd  
assign b = gnd; //Connect b to gnd
```

# Signal Strengths

- Verilog's logic system has logic values and logic strengths
- The strength of a signal refers to the ability to act as a driver determining the resultant logic value on a net
  - gives additional information that determines the result of contending drivers on a net when multiple drives are present, or when the nets are modeled as charge storage capacitors
- The signals in gate-level models are “strong” by default



# STRENGTHS

| <u>Strength Name</u> | <u>Strength Level</u> | <u>Element Modelled</u>                | <u>Declaration Abbreviation</u> |
|----------------------|-----------------------|--|---------------------------------|
| Supply Drive         | 7                     | Power supply connections.              | supply                          |
| Strong Drive         | 6                     | Default gate & assign output strength. | strong                          |
| Pull Drive           | 5                     | Gate & assign output strength.         | pull                            |
| Large Capacitor      | 4                     | Size of trireg net capacitor.          | large                           |
| Weak Capacitor       | 3                     | Gate & assign output strength.         | weak                            |
| Medium Capacitor     | 2                     | Size of trireg net capacitor.          | medium                          |
| Small Capacitor      | 1                     | Size of trireg net capacitor.          | small                           |
| High Impedence       | 0                     | Not Applicable.                        | highz                           |

**Output-side strength levels for different input-side strength values of rnmoss, rpmoss, and rcmos switches**

| Input strength      | Output strength     |
|---------------------|---------------------|
| Supply – drive      | Pull – drive        |
| Strong – drive      | Pull – drive        |
| Pull – drive        | Weak – drive        |
| Weak – drive        | Medium – capacitive |
| Large – capacitive  | Medium – capacitive |
| Medium – capacitive | Small – capacitive  |
| Small – capacitive  | Small – capacitive  |
| High impedance      | High impedance      |



# **TIME DELAYS WITH SWITCH PRIMITIVES**



# 1. MOS and CMOS switches

| Switch Element           | Delay Specification                             | Examples   |
|--------------------------|---|--|
| pmos, nmos, rpmos, rnmos | Zero (no delay)                                 | pmos p1(out, data, control);   |
|                          | One (same delay on all transitions)             | pmos #(1) p1(out, data, control);  |
|                          | Two (rise, fall)                                | nmos #(1, 2) p2(out, data, control);   |
|                          | Three (rise, fall, turnoff)                     | nmos #(1, 3, 2) p2(out, data, control);  |
| cmos, rcmos              | Zero, one, two, or three delays (same as above) | cmos #(5) c2(out, data, nctrl, pctrl);<br><br>cmos #(1,2) c1(out, data, nctrl, pctrl); |

## 2. Bidirectional pass switches

| Switch Element                      | Delay Specification   | Examples  |
|-------------------------------------|---|---|
| tran, rtran                         | No delay specification allowed  |   |
| tranif1, rtranif1 tranif0, rtranif0 | Zero (no delay)<br><br>One (both turn-on and turn-off)<br><br>Two (turn-on, turn-off) | rtranif0 rt1(inout1, inout2, control);<br><br>tranif0 #(3) T(inout1, inout2, control);<br><br>tranif1 #(1,2) t1(inout1, inout2, control); |

# 1. Verilog Model for CMOS Inverter

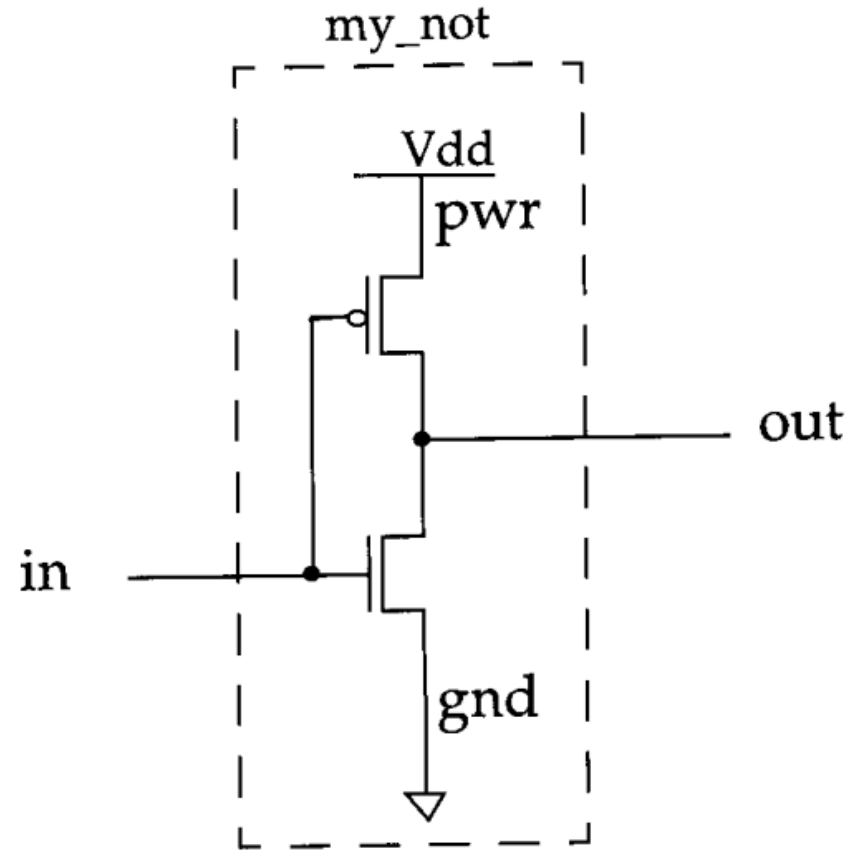 

```
//Define an inverter using MOS switches
module my_not(out, in);



output out;
input in;

//declare power and ground
supply1 pwr;
supply0 gnd;

//instantiate nmos and pmos switches
pmos (out, pwr, in);
nmos (out, gnd, in);

endmodule
```

## 2. CMOS NOR gate

  



```

//Define our own nor gate, my_nor
module my_nor(out, a, b);

output out;
input a, b;

//internal wires
wire c;

//set up power and ground lines
supply1 pwr;      //pwr is connected to Vdd (power supply)
supply0 gnd ;     //gnd is connected to Vss(ground)


//instantiate pmos switches
pmos  (c, pwr, b);
pmos  (out, c, a);

//instantiate nmos switches
nmos  (out, gnd, a);
nmos  (out, gnd, b);


endmodule

```

### 3. 3-input nand Gate

 

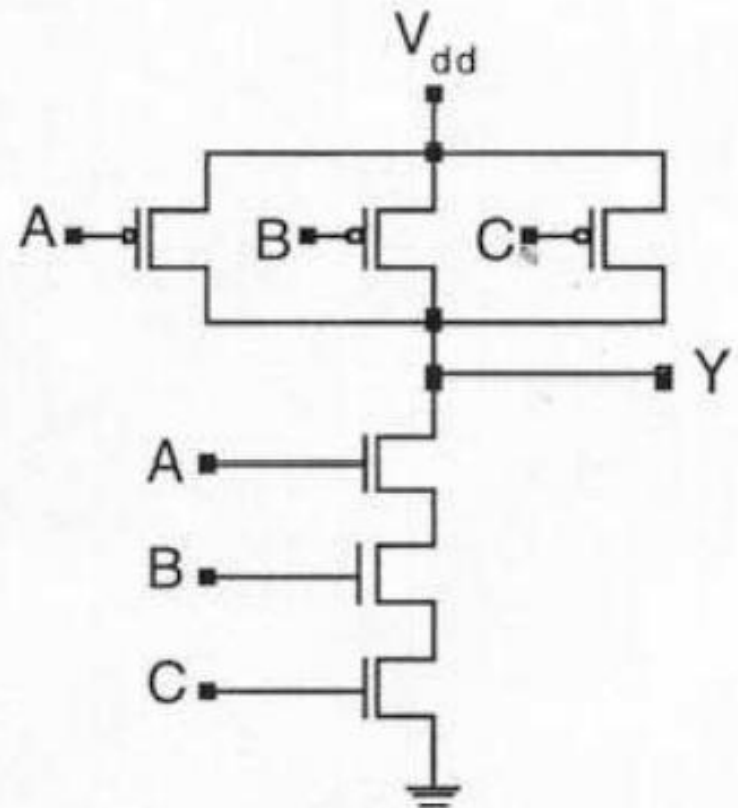
```
module nand_3 (Y, A, B, C);  
  output      Y;  
  input       A, B, C;  
  supply0     GND;  
  supply1     PWR;  
  wire        w1, w2;  
  
  pmos        (Y, PWR, A);  
  pmos        (Y, PWR, B);  
  pmos        (Y, PWR, C);  
  nmos        (Y, w1, A);  
  nmos        (w1, w2, B);  
  nmos        (w2, GND, C);  
endmodule
```


 
# 4. 2-input nand Gate using nmos

- nmos pull-down logic + depletion load pull-up device

```
module nmos_nand_2 (Y, A, B);  
  output      Y;  
  input       A, B;  
  supply0     GND;  
  → tri       w1;  
  
  pullup      (Y);  
  nmos        (Y, w1, A);  
  nmos        (w1, GND, B);  
endmodule
```





**THANK YOU**